

# Transistor Amplifier Simplified

This presentation tries to clear the concept of a  
**Transistor Amplifier.**


*Please Note: Some ideas are over-simplified to  
understand the main concept.*

**Author: Prasad Mehendale**

**Feel free to distribute this file to others.**


**Your questions and suggestions are welcome.**

# Resistance Potential Divider

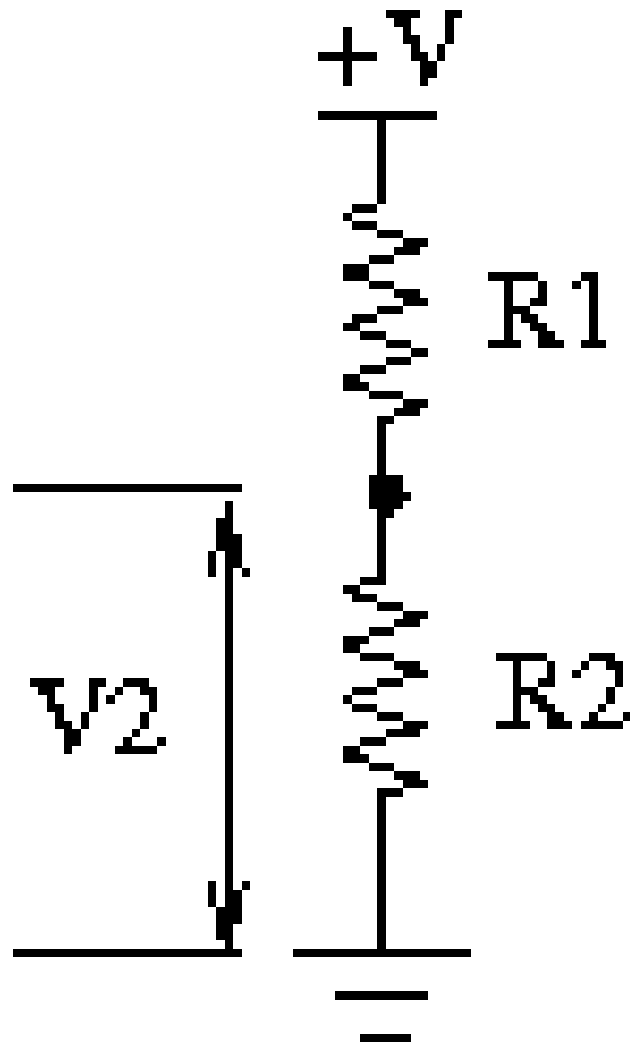


- $V_2 = (V * R_2) / (R_1 + R_2)$
- So, more is the value of  $R_2$ , more is the voltage drop across it.

# Transistor: Transferred Resistor-1

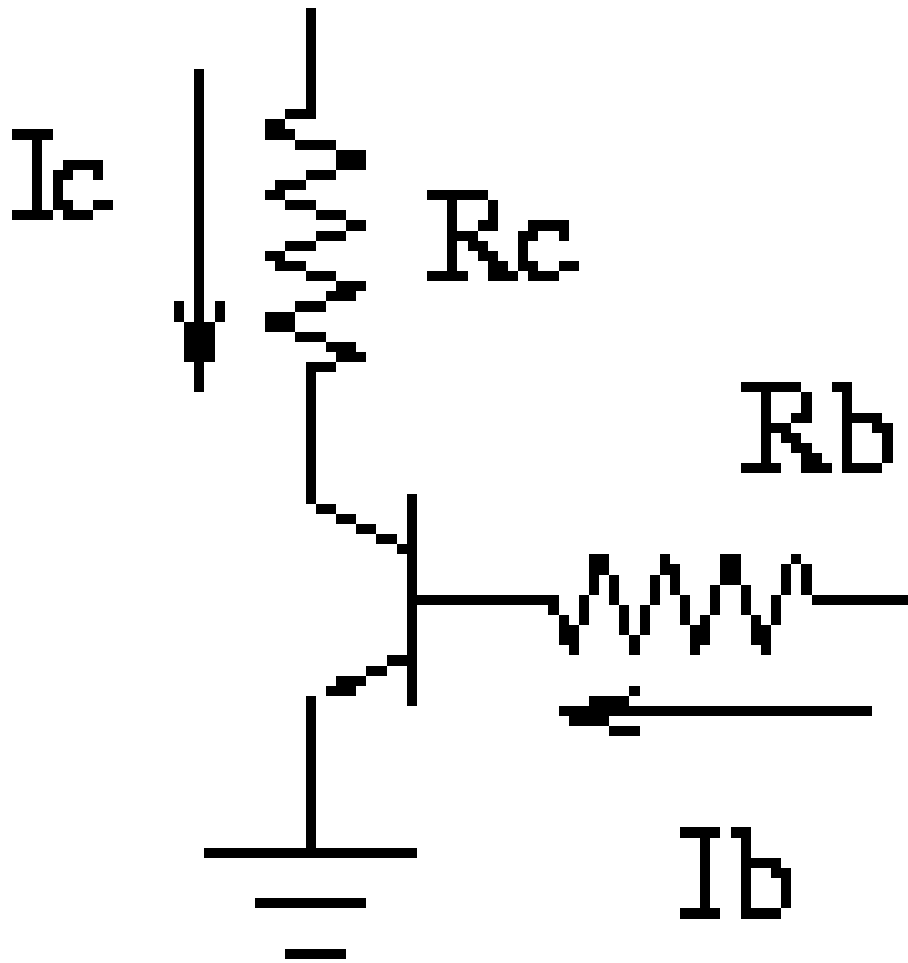

- When you increase the base current, collector to emitter current increases
- It means, Collector to emitter resistance decreases.


# Transistor: Transferred Resistor-2

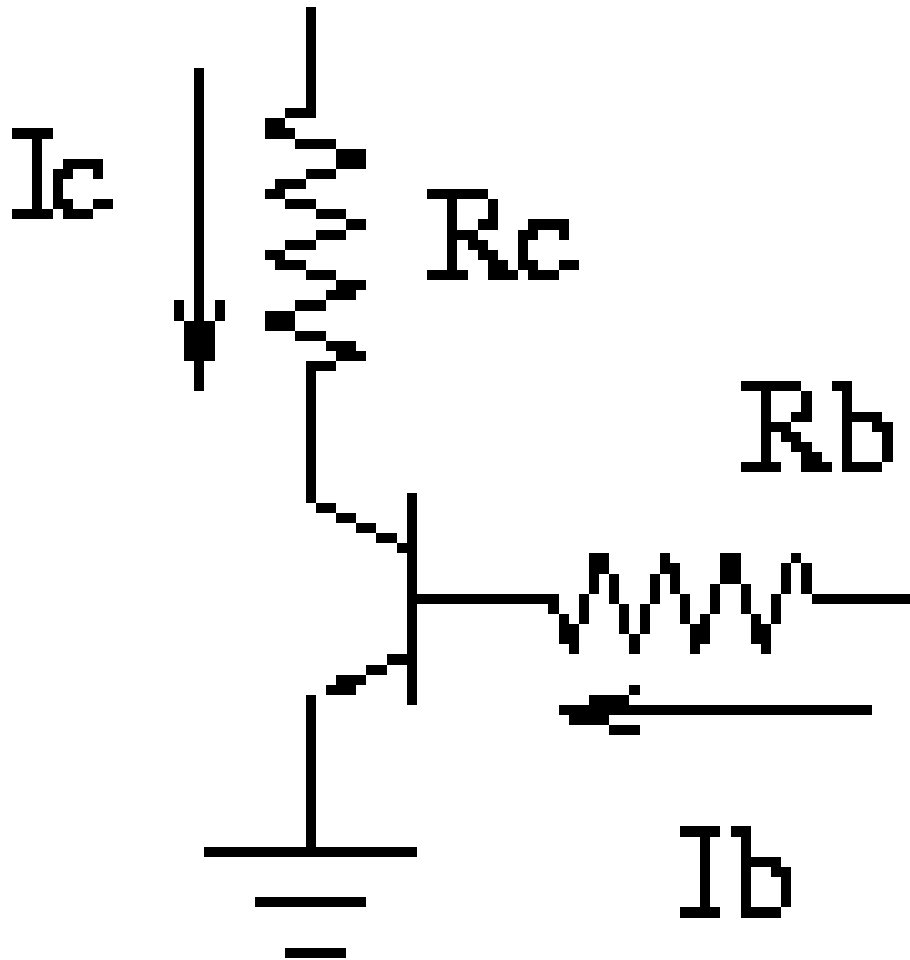


- When base current decreases, collector current also decreases.
- It means, Collector to Emitter resistance increases.
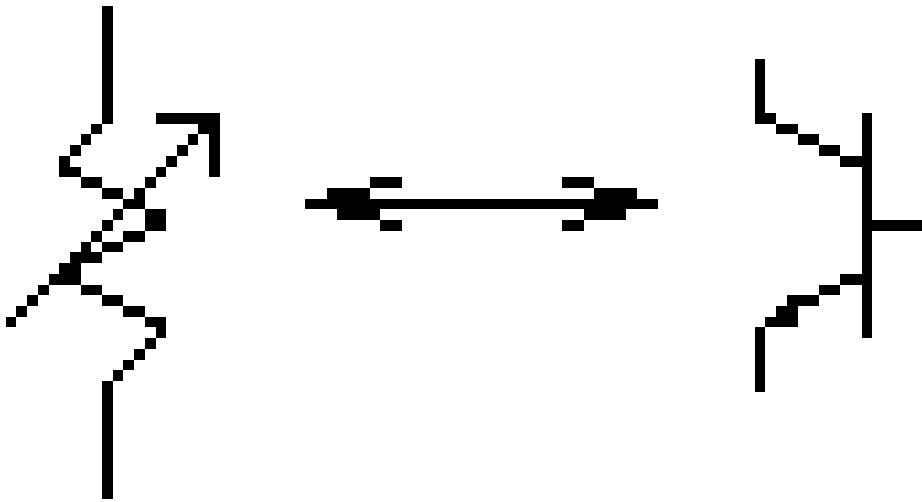
# Transistor: Electrically Variable Resistor

- So transistor can be considered as an electrically variable resistor.
- More is the base current, lesser is the resistance of CE region and vice versa.




# Potential Divider (again...)

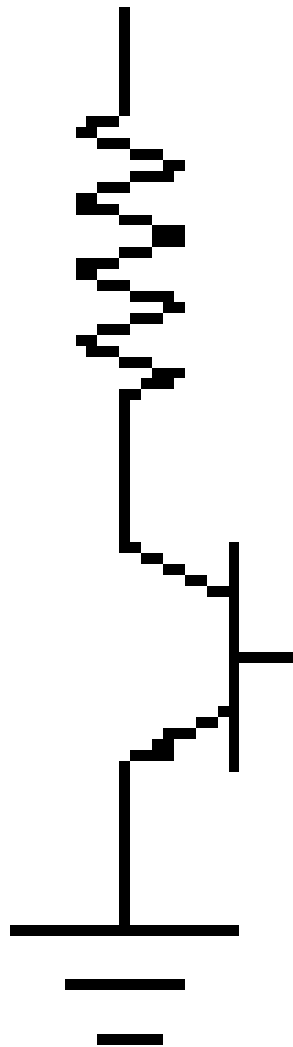


- Imagine the transistor in series with the collector-emitter resistor.
- The resistance and the transistor now form the potential divider

# The “Load Line” - 1

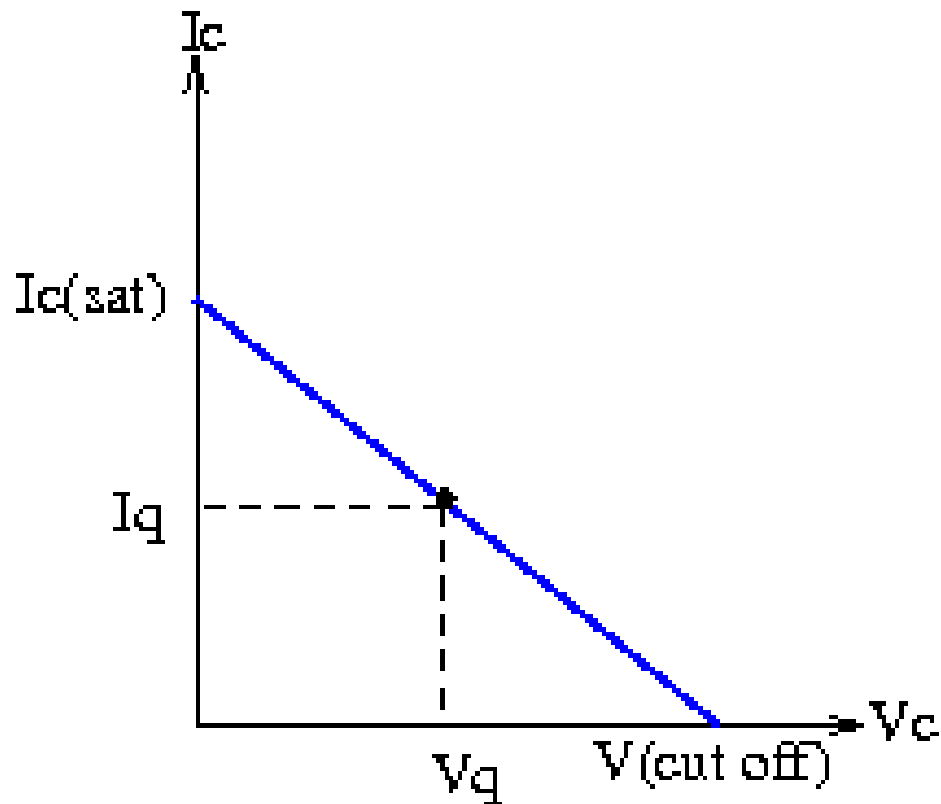

- When transistor is full of majority carriers, it is saturated with the majority carriers.
- So “saturated” current flows through the transistor, from collector to emitter.
- This is  **$I_c(\text{sat})$**


# The “Load Line” - 2

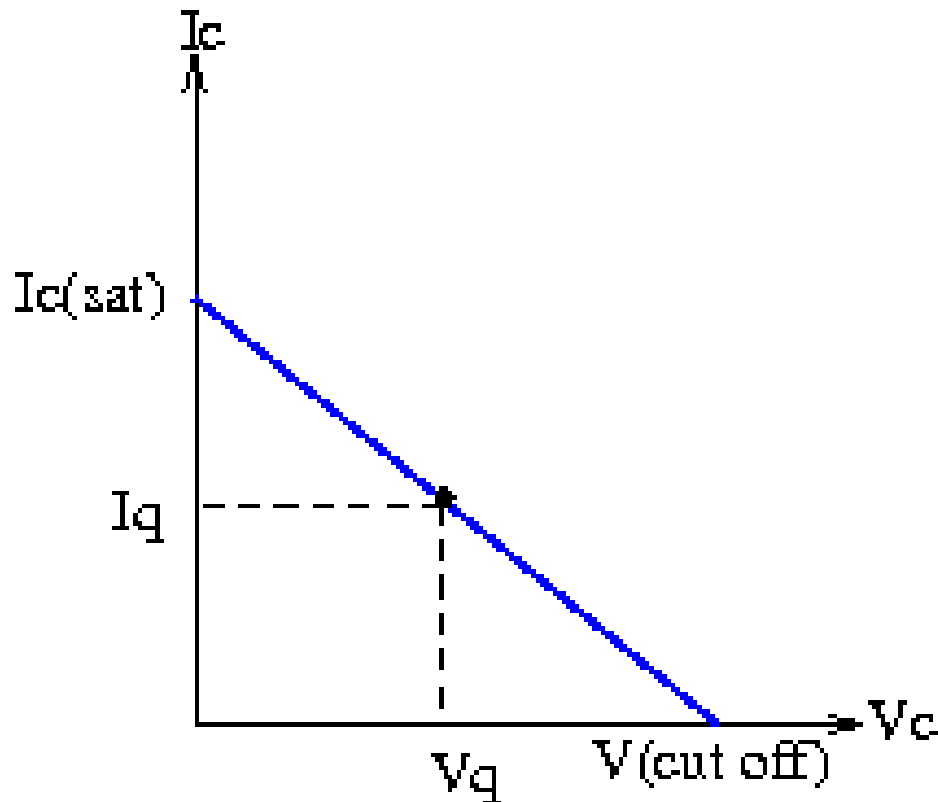

- When no current is injected in to the base, there are no majority carriers in the collector-emitter region so the transistor is open.
- Collector voltage is maximum.
- **This is cut-off condition**



# The “Load Line” - 3

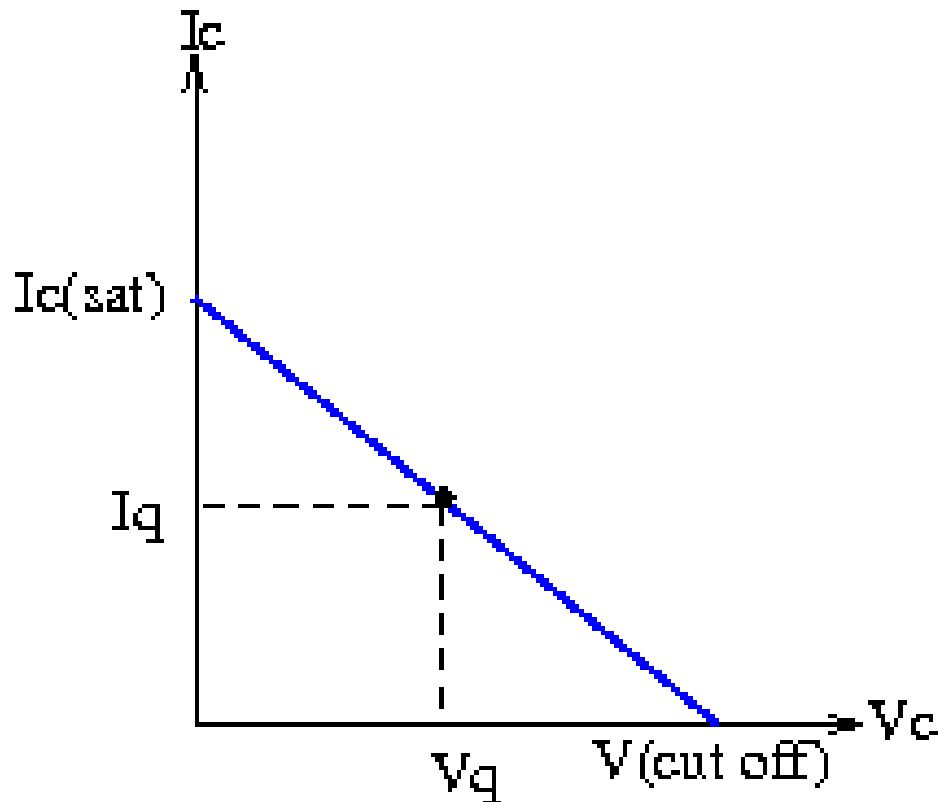


- Straight line between  $I_c(\text{sat})$  and  $V(\text{cut-off})$  is known as

## **The “Load Line”**


- **The point on the load line with coordinates  $(V_q, I_q)$  is called the Quiescent point.**

# The “Quiescent Point”

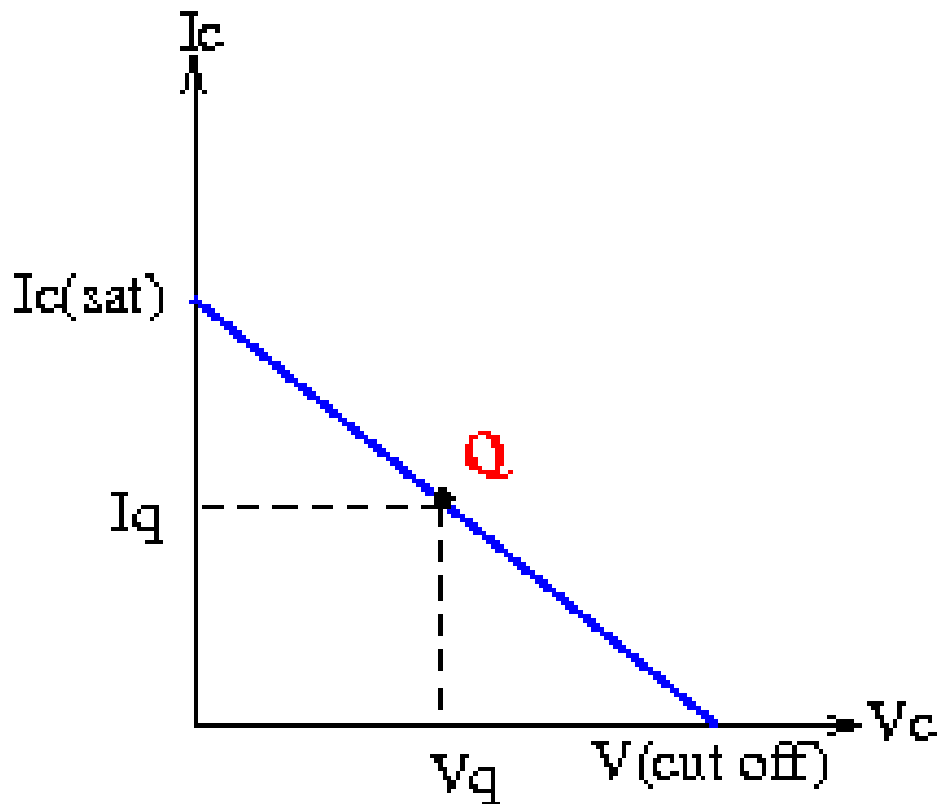


- Quiescent means QUIET.
- At the transistor base, no ac signal is applied
- Only the biasing voltage exists
- $I_q$  and  $V_q$  are fixed, so the state is “**quiet**”

# The Transistor Signalled ! -1

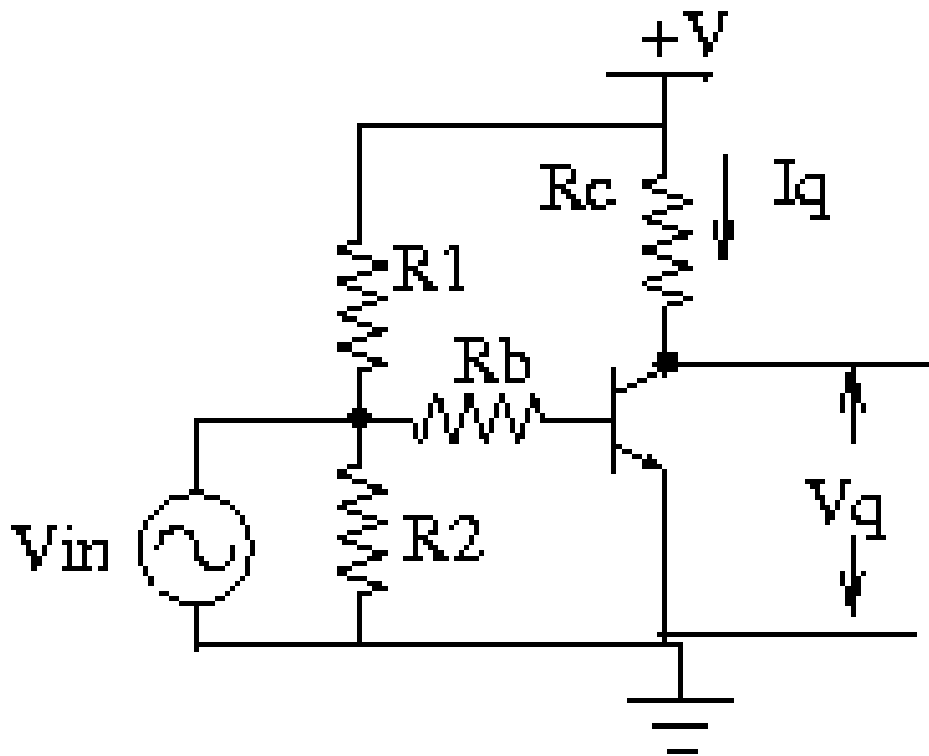


- $R_1$ - $R_2$  is potential divider biasing circuit.
- Voltage across  $R_2$  is such that it injects current  $I_b$  through  $R_b$  to draw collector current  $I_q$  & Collector voltage =  $V_q$
- $V_{in}$  is the external ac signal applied.

# The Transistor Signalled ! - 2

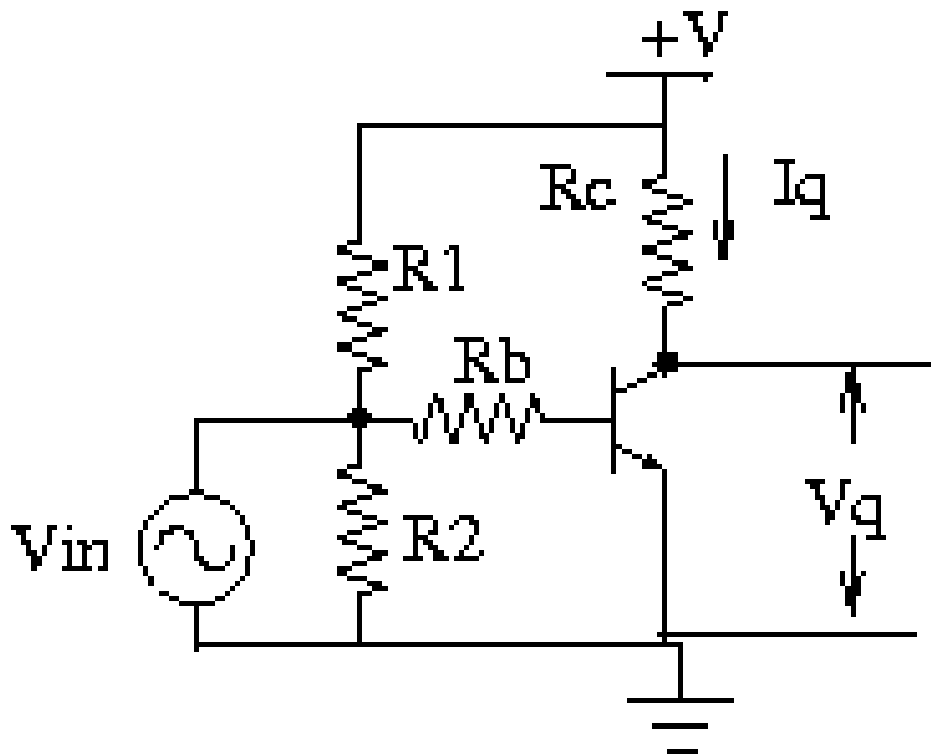


- $V_{in}$  changes w.r.t. Time.
- This changes  $I_b$
- Continuous change in  $I_b$  results in change in  $I_q$  and  $V_q$ .

# The Transistor **Signaled** ! - 3

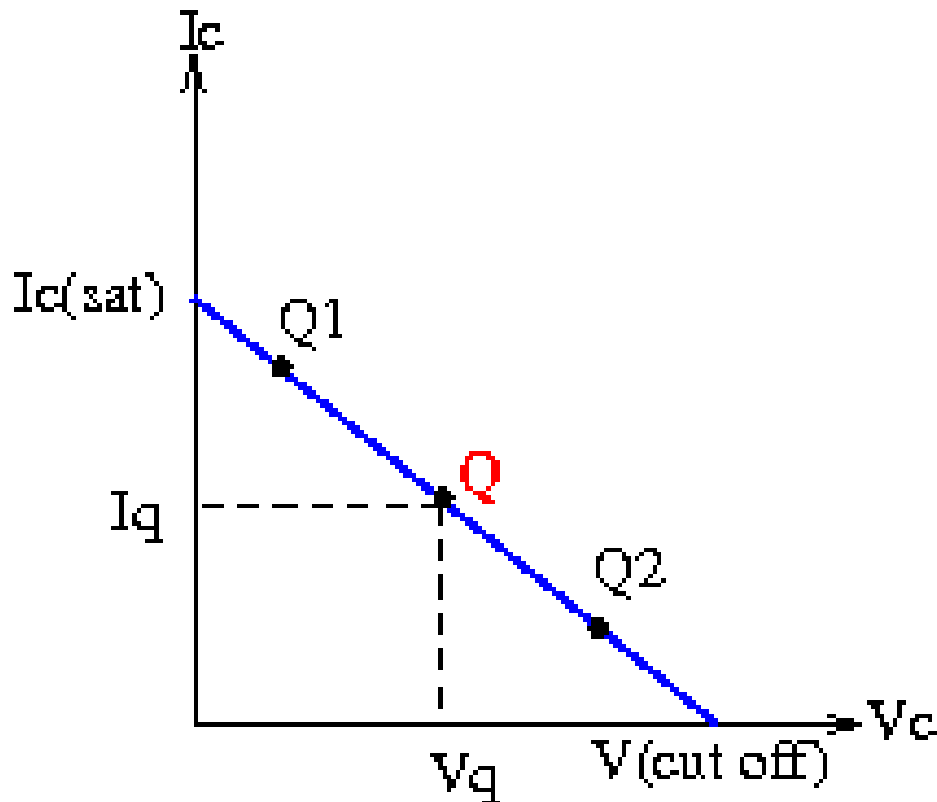


- When  $I_b$  increases, point  $Q$  changes to  $Q_1$ . It can go up to  **$I_c(\text{sat})$** .
- When  $I_b$  decreases, point  $Q$  changes its position to  $Q_2$ . It can go down to  **$V(\text{cut off})$**
- As the  **$V_{in}$**  signal changes continuously, The  $Q$  point can take a journey from  **$I_c(\text{sat})$**  to  **$V(\text{cut off})$**  and back.

# Amplification -1

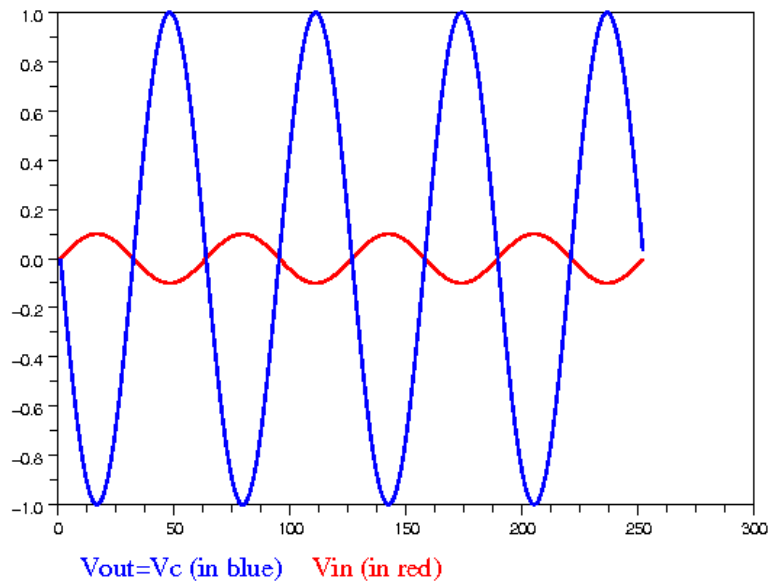


- Small changes in  $V_{in}$  are in mV.
- This results in the change the  $V_q$  such that  $V_q$  changes from 0 to  $V(\text{cut-off})$ .  $V(\text{cut-off})$  is in volts.
- Thus small change in  $V_{in}$  results in large change in  $V_c$ , keeping the wave shape the same.
- $V(\text{in})$  is in red
- $V(\text{out})=V_c$  in blue

# Note the following:

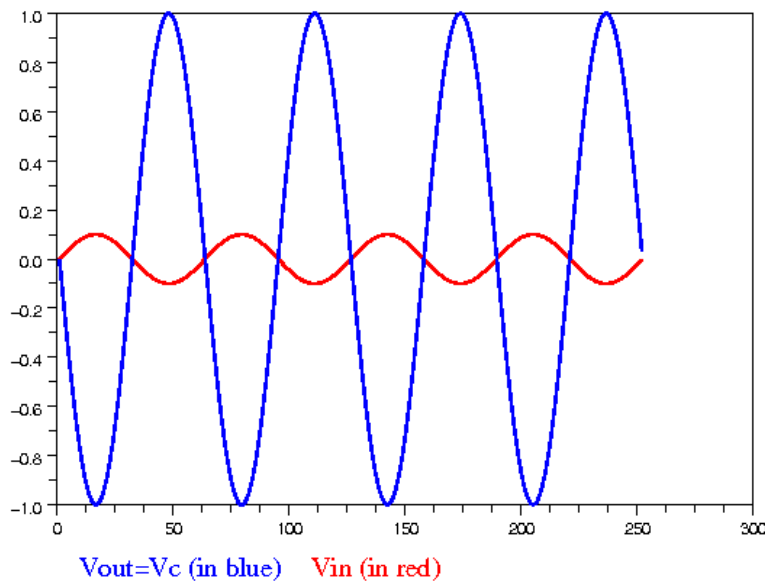

- $V_{in}$  is small
- $V_c = V_{out}$  is large
- $V_c$  lags behind  $V_{in}$  by 180 deg because, when  $I_b$  increases, “resistance” between collector and emitter decreases.
- $V(in)$  is in red
- $V(out) = V_c$  in blue

# Note the following:

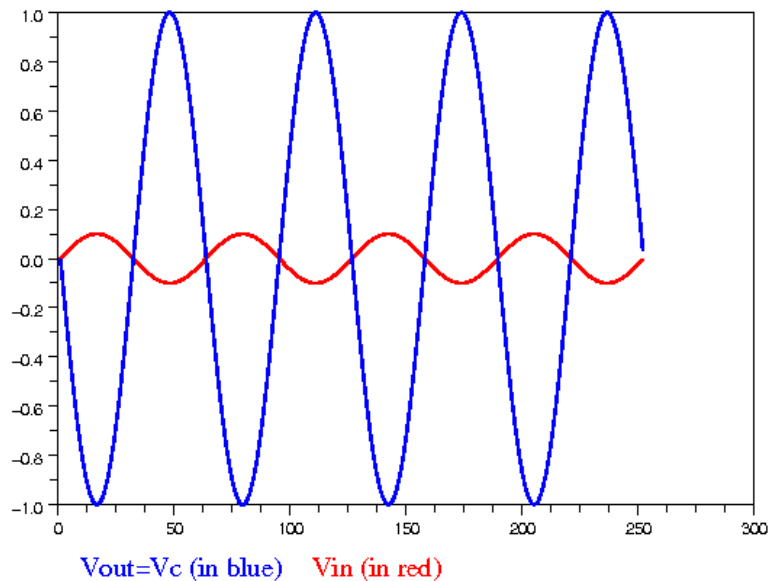

- Amplifier increases the magnitude of input voltage
- Amplifier maintains the wave shape for the output
- Output wave-shape is shifted by 180 deg.